



UNIVERSITY OF PISA

DEPARTMENT OF INFORMATION ENGINEERING

Master's Degree in Computer Engineering

Electronics and Communications Systems

Linear Interpolator

Design and Implementation

VHDL Digital Design for FPGA

Professors:

Luca Fanucci
Pietro Nannipieri
Tommaso Bocchi

Student:

Luca Rotelli

ACADEMIC YEAR 2025/2026

March 25, 2026

Contents

1	Introduction	3
1.1	Problem Statement	3
1.2	Interface	3
2	State of the Art	4
2.1	Zero-Order Hold	4
2.2	Linear Interpolation	4
2.3	Higher-Order Polynomial and Spline Methods	4
2.4	FIR, Polyphase, and Farrow Structures	5
2.5	Hardware Considerations	5
2.6	Motivation for the Selected Architecture	5
3	Architecture	6
3.1	Overview	6
3.2	Block Diagram	6
3.3	Operation Principle	7
3.4	Arithmetic Precision	7
3.5	Pipeline Latency	7
4	VHDL Implementation	8
4.1	Entity Declaration	8
4.1.1	Port Description	8
4.1.2	Generic Parameters	8
4.2	Architecture Structure	8
4.2.1	Signal Declarations	9
4.3	Synchronous Process	9
4.4	Combinatorial Datapath	9
4.4.1	Arithmetic Details	10
4.5	Design Considerations	10
4.5.1	Overflow Prevention	10
4.6	State Machine	11
5	Verification	12
5.1	Test Strategy	12
5.1.1	Validation Scenarios	12
5.2	Test Cases	12
5.3	Verification Methodology	14
5.3.1	Testbench Structure	14
5.3.2	Coverage Metrics	15
5.4	Simulation Results	15
5.4.1	Waveform Analysis	15
5.4.2	Numerical Verification Examples	16
5.4.3	Performance Metrics	17
6	Synthesis Results	18
6.1	Target Device	18
6.2	Resource Utilization	18
6.3	Timing Analysis	18
6.3.1	Maximum Operating Frequency Calculation	19
6.3.2	I/O Register Barrier	19
6.4	Power Consumption	20

6.4.1	Power Analysis	20
6.5	Implementation Quality	21
6.5.1	Critical Path Analysis	22
7	Conclusions	23
7.1	Project Summary	23

1 Introduction

1.1 Problem Statement

Design a digital circuit that, given an input signal sampled with a sampling period of T , produces a linearly interpolated version of the input signal as output. Use an interpolation factor $L = 4$: for each input sample, the interpolator system must insert other $L - 1$ samples.

The interpolation is computed using the formula:

$$y(nT + uT) = (y_{n+1} - y_n)u + y_n$$

where $u = \frac{k}{L}$ with $k \in \{0, 1, \dots, L - 1\}$.

1.2 Interface

The circuit interface is defined as follows:

 


Figure 1: Linear Interpolator Interface

- **clk**: System clock
- **rst_n**: Active-low asynchronous reset
- **din[15:0]**: 16-bit signed input sample
- **dout[15:0]**: 16-bit signed interpolated output

2 State of the Art

Interpolation is a fundamental operation in digital signal processing whenever the sampling rate of a discrete-time signal must be increased. Typical application domains include audio processing, sensor-data conditioning, communication systems, control loops, and FPGA-based preprocessing chains. In all these scenarios, the objective is to reconstruct additional samples between two consecutive input values so that the generated sequence is a better approximation of the original continuous-time signal.

In practice, the state of the art includes several interpolation strategies, each characterized by a different trade-off between waveform quality, hardware complexity, resource occupation, power consumption, and timing performance. For an FPGA-oriented design such as the one developed in this project, the most relevant comparison is not only mathematical accuracy, but also implementation cost and ease of verification.

2.1 Zero-Order Hold

The simplest possible solution is the **zero-order hold** (ZOH), also known as sample repetition. In this method each input sample is repeated for L output periods, producing a staircase waveform. Its main advantage is extremely low hardware cost, since no arithmetic datapath is required and the implementation can be based almost entirely on registers and control logic.

However, zero-order hold does not perform a true interpolation between adjacent samples. The output remains constant until the next sample arrives, creating discontinuities and stronger spectral images. For this reason, it is usually considered a low-cost baseline rather than a high-quality interpolation method.

2.2 Linear Interpolation

Linear interpolation is one of the most common solutions when a good compromise between quality and complexity is required. The method reconstructs the intermediate values along the straight line joining two consecutive samples:

$$y\left(nT + \frac{k}{L}T\right) = y_n + \frac{k}{L}(y_{n+1} - y_n), \quad k \in \{0, 1, \dots, L-1\}.$$

Compared with zero-order hold, linear interpolation produces a smoother output waveform and eliminates the discontinuity at the sample boundaries. From a hardware point of view, it remains compact because it only requires subtraction, multiplication by a small factor, division by the interpolation factor, and final accumulation. When L is a power of two, the division can be implemented through an arithmetic right shift instead of a generic divider, which makes the method particularly suitable for fixed-point FPGA implementations.

Its limitation is that it is still a first-order approximation. The waveform is continuous, but the slope changes abruptly at the original sample instants. Even so, for a fixed interpolation factor such as $L = 4$, linear interpolation is often the preferred engineering choice when the goal is an efficient and reliable implementation rather than maximum reconstruction accuracy.

2.3 Higher-Order Polynomial and Spline Methods

When improved smoothness is required, designers may adopt quadratic, cubic, or spline-based interpolation. These techniques exploit more than two neighboring samples and reconstruct the missing points using higher-order polynomials. Their main benefit is reduced approximation error and a smoother derivative profile, which is useful in applications such as image processing, motor control, and high-fidelity audio systems.

The drawback is a much higher implementation cost. More samples must be stored, the control logic becomes more articulated, and the arithmetic datapath requires additional multipliers

and adders. On FPGA platforms this often leads to greater LUT usage, more registers, and in many cases dedicated DSP blocks. Therefore, these techniques are justified only when the extra output quality is necessary.

2.4 FIR, Polyphase, and Farrow Structures

The most accurate family of solutions for interpolation and resampling is based on **FIR filtering**. The classical multirate approach inserts additional samples and then applies a low-pass interpolation filter. In efficient digital hardware, this concept is usually implemented through **polyphase** structures, which avoid unnecessary operations and provide a clean architecture for fixed-rate interpolation.

For more advanced cases, especially fractional-delay or variable-rate conversion, **Farrow** structures are also widely used. These architectures are very flexible and can offer excellent spectral performance, but they are significantly more expensive in terms of datapath complexity, coefficient management, and verification effort. For a compact educational project with fixed $L = 4$, these approaches would be disproportionate with respect to the required functionality.

2.5 Hardware Considerations

Independent of the selected interpolation law, FPGA implementations usually have to address three key issues:

- **Area efficiency:** low-cost designs prefer compact datapaths and resource sharing over fully parallel solutions.
- **Fixed-point robustness:** intermediate operations such as $(y_{n+1} - y_n) \cdot k$ require extra bits to avoid overflow and preserve the sign correctly.
- **Timing closure:** registering the output and keeping the architecture simple improves the probability of meeting the target clock period.

For this reason, many practical interpolators are implemented as sequential architectures controlled by a small counter or finite-state machine. Such solutions reuse the same arithmetic resources across several clock cycles, reducing area while still producing one output sample per cycle.

2.6 Motivation for the Selected Architecture

Considering the project specifications, linear interpolation represents the most appropriate solution. It offers a substantial improvement over zero-order hold, while avoiding the complexity of polynomial, spline, or FIR-based interpolators. In particular, the fixed interpolation factor $L = 4$ makes the architecture especially convenient because division by L can be reduced to a simple arithmetic shift.

The adopted design follows a sequential, time-multiplexed approach: two registers store consecutive samples, a 2-bit counter identifies the interpolation phase, and a compact combinational datapath computes the intermediate value. This solution matches the state of the art for low-cost FPGA implementations, where the preferred strategy is to select the simplest architecture that fully satisfies the specification with adequate numerical precision, limited resource usage, and good timing behavior.

3 Architecture

3.1 Overview

The interpolator uses a simple sequential architecture with:

- Four registers to store current (y_n), next (y_{n+1}) samples, counter state, and output
- A 2-bit counter cycling from 0 to L-1
- Combinatorial arithmetic logic for interpolation computation
- Output register for proper timing closure and reg-to-reg paths

3.2 Block Diagram

 


Figure 2: Functional block diagram of the linear interpolator with symbol legend

The design consists of the following functional blocks:

1. **Sample Registers:** Two 16-bit signed registers ('r_y_curr', 'r_y_next') hold consecutive input samples
2. **Interpolation Counter:** 2-bit register ('r_counter') cycles from 0 to 3, controlling interpolation phase
3. **Arithmetic Unit:** Combinatorial datapath computes $(y_{n+1} - y_n) \cdot k/L + y_n$ using 20-bit internal precision
4. **Output Register:** 16-bit register ('r_dout') holds the computed interpolated value for timing closure

3.3 Operation Principle

The interpolator works as follows:

1. Counter ‘r_counter’ cycles every clock: $0 \rightarrow 1 \rightarrow 2 \rightarrow 3 \rightarrow 0 \rightarrow 1 \rightarrow 2 \rightarrow 3 \dots$
2. When counter wraps reach 3, capture new input sample:
 - Shift registers: ‘r_y_curr’ $\leftarrow$ ‘r_y_next’
 - Load new sample: ‘r_y_next’ $\leftarrow$ ‘din’
3. For each counter value k, compute interpolated output (combinatorial):
 - Calculate difference: $\Delta = y_{n+1} - y_n$ (17-bit signed)
 - Multiply by k: $temp = \Delta \cdot k$ (20-bit signed)
 - Divide by L=4: $result = temp \gg 2$ (arithmetic right shift)
 - Add offset: $y_i = result + y_n$ (20-bit)
 - Truncate to 16-bit: extract lower N bits
4. Register output: ‘r_dout’ $\leftarrow y_i$ (every clock cycle)
5. Drive output port: ‘dout’ $\leftarrow$ ‘r_dout’

3.4 Arithmetic Precision

The computation uses extended precision internally to prevent overflow:

- **Input samples:** 16-bit signed (N bits), range $[-32768, 32767]$
- **Difference Δ :** 17-bit signed ($N + 1$ bits) via sign extension
- **Counter k:** 2-bit unsigned, extended to 3-bit signed for multiplication
- **Multiplication $\Delta \times k$:** 20-bit signed ($N + 3$ bits)
 - Maximum: $65535 \times 3 = 196605$ fits in 20-bit range (± 524287)
- **Division by 4:** Arithmetic right shift by 2 (maintains sign, 20-bit result)
- **Final sum:** 20-bit addition with sign-extended ‘r_y_curr’
- **Output:** Lower 16 bits extracted

This approach handles the worst-case intermediate arithmetic without overflow in the internal datapath. No explicit saturation stage is implemented at the output; instead, the registered result is obtained from the 16-bit slice used by the RTL.

3.5 Pipeline Latency

The design has a **1-cycle output latency** due to the output register:

- Clock N: Counter and sample registers updated, interpolation computed combinatorially
- Clock N+1: Result captured in ‘r_dout’ and appears on ‘dout’ port
- Total delay: Interpolation values appear 1 clock after counter changes

4 VHDL Implementation

4.1 Entity Declaration

The main entity that contains all the components and defines the interface of the linear interpolator:

```
1 entity linear_interpolator is
2   generic (
3     N : integer := 16 -- data width
4   );
5   port (
6     clk : in std_logic;
7     rst_n : in std_logic;
8     din : in std_logic_vector(N-1 downto 0);
9     dout : out std_logic_vector(N-1 downto 0)
10  );
11 end entity linear_interpolator;
```

4.1.1 Port Description

- **clk**: System clock input - all operations are synchronous to rising edge
- **rst_n**: Asynchronous active-low reset - initializes all registers
- **din**: 16-bit `std_logic_vector` input carrying a signed sample in two's complement format
- **dout**: 16-bit `std_logic_vector` output carrying the interpolated signed sample in two's complement format

Although the external interface uses `std_logic_vector`, the datapath internally converts the samples to **signed** values through the `numeric_std` package in order to perform the interpolation arithmetic correctly.

4.1.2 Generic Parameters

- **N**: Data width in bits (default 16) - allows design flexibility

In the current implementation the interpolation factor is fixed to $L = 4$. This choice is directly reflected in the 2-bit counter and in the division-by-4 stage implemented through arithmetic right shift.

4.2 Architecture Structure

The architecture is organized into distinct functional blocks:

 


Figure 3: Schematic View of Linear Interpolator RTL

4.2.1 Signal Declarations

Internal registers:

```
1 signal r_y_curr    : signed(N-1 downto 0);    -- Current sample yn
2 signal r_y_next    : signed(N-1 downto 0);    -- Next sample yn+1
3 signal r_counter    : unsigned(1 downto 0);    -- 2-bit counter (0-3)
4 signal r_dout       : signed(N-1 downto 0);    -- Output register
```

Combinatorial signals for arithmetic datapath (20-bit precision):

```
1 signal s_diff       : signed(N downto 0);      -- 17-bit difference
2 signal s_counter_signed : signed(2 downto 0);  -- 3-bit signed k
3 signal s_mult_res    : signed(N+3 downto 0);   -- 20-bit mult result
4 signal s_div_res     : signed(N+3 downto 0);   -- 20-bit div result
5 signal s_sum_final   : signed(N+3 downto 0);   -- 20-bit final sum
```

4.3 Synchronous Process

The main synchronous process handles sample storage, counter, and output register:

```
1 process(clk, rst_n)
2 begin
3     if rst_n = '0' then
4         r_y_curr    <= (others => '0');
5         r_y_next    <= (others => '0');
6         r_counter    <= "00";
7         r_dout       <= (others => '0');
8     elsif rising_edge(clk) then
9         -- Update counter and sample registers
10        if r_counter = "11" then -- L-1 = 3
11            r_counter <= "00";
12            r_y_curr  <= r_y_next;
13            r_y_next  <= signed(din);
14        else
15            r_counter <= r_counter + 1;
16        end if;
17
18        -- Register output for timing closure
19        r_dout <= s_sum_final(N-1 downto 0);
20    end if;
21 end process;
```

Key features:

- Asynchronous reset clears all registers
- Counter cycles 0 to L-1
- Sample shift occurs when counter wraps
- New input captured synchronously

4.4 Combinatorial Datapath

The arithmetic computation is implemented combinatorially with manual sign extension and 20-bit precision:

```

1  -- 1. Counter extension to signed 3-bit
2  s_counter_signed <= signed('0' & std_logic_vector(r_counter));
3
4  -- 2. Difference calculation (17-bit signed)
5  s_next_ext <= r_y_next(N-1) & r_y_next; -- Sign extend
6  s_curr_ext <= r_y_curr(N-1) & r_y_curr;
7  s_diff      <= s_next_ext - s_curr_ext;
8
9  -- 3. Multiplication (17-bit * 3-bit = 20-bit)
10 s_mult_res <= s_diff * s_counter_signed;
11
12 -- 4. Division by 4 (arithmetic right shift by 2)
13 s_sign_bit <= s_mult_res(N+3); -- Extract sign
14 s_div_res <= s_sign_bit & s_sign_bit & s_mult_res(N+3 downto 2);
15
16 -- 5. Extend current sample to 20-bit
17 s_curr_final_ext <= r_y_curr(N-1) & r_y_curr(N-1) &
18                      r_y_curr(N-1) & r_y_curr(N-1) & r_y_curr;
19 -- 6. Add offset yn (20-bit addition)
20 s_sum_final <= s_curr_final_ext + s_div_res;
21
22 -- 7. Output assignment (registered in synchronous process)
23 dout <= std_logic_vector(r_dout);

```

4.4.1 Arithmetic Details

1. **Manual Sign Extension:** Inputs extended by concatenating MSB for signed arithmetic
2. **17-bit Difference:** $(y_{n+1} - y_n)$ with one extra sign bit
3. **3-bit Counter:** 2-bit unsigned counter extended to 3-bit signed (0-3 range)
4. **20-bit Multiplication:** $17 \times 3 = 20$ bits, sufficient for range ± 196605
5. **Arithmetic Shift:** Right shift by 2 with sign replication implements division by 4
6. **20-bit Addition:** Current sample sign-extended to 20 bits, added to shifted result
7. **Truncation:** Lower 16 bits extracted for output, with no explicit saturation stage
8. **Output Register:** Result registered for proper reg-to-reg timing paths

4.5 Design Considerations

4.5.1 Overflow Prevention

The extended precision arithmetic prevents overflow:

- 16-bit inputs can produce 17-bit difference
- Multiplication produces up to 20-bit result
- Arithmetic right shift preserves sign
- Final addition fits within 20-bit range

4.6 State Machine

The design operates in a simple cyclic pattern:

- State 0 (k=0): Output y_n
- State 1 (k=1): Output $y_n + \frac{1}{4}(y_{n+1} - y_n)$
- State 2 (k=2): Output $y_n + \frac{2}{4}(y_{n+1} - y_n)$
- State 3 (k=3): Output $y_n + \frac{3}{4}(y_{n+1} - y_n)$

After state 3, the counter wraps to 0, samples shift (y_{n+1} becomes new y_n), and a new input sample is captured as y_{n+1} .

5 Verification

5.1 Test Strategy

A comprehensive testbench was developed to verify all aspects of the design. The verification approach includes:

- Directed tests for specific functionality
- Corner case testing (boundary values, edge conditions)
- Sign handling verification (positive, negative, mixed)
- Arithmetic accuracy checking

The testbench verifies:

- **Reset functionality:** Proper initialization of all registers
- **First sample handling:** Correct behavior on initial input
- **Normal interpolation:** Linear interpolation between positive values
- **Dead zone cases:** Identical input samples (zero difference)
- **Negative value transitions:** Interpolation with negative numbers
- **Large step transitions:** Maximum difference between samples
- **Boundary conditions:** Min/max value handling
- **Sign preservation:** Correct sign through computation
- **Output range verification:** Correct behavior under extreme transitions with the implemented truncation-based output stage

5.1.1 Validation Scenarios

The verification campaign can be grouped into three macro-scenarios:

- **Initial behavior:** reset release, first-sample loading, and startup evolution before a full interpolation cycle is available
- **Nominal behavior:** positive ramps, negative ramps, sign changes, and standard sample-to-sample transitions
- **Boundary and stress behavior:** dead-zone cases, very small differences, large steps, and extreme signed transitions close to the numerical limits

5.2 Test Cases

Key test scenarios implemented:

1. Test 1 - Reset Behavior

- Apply asynchronous reset
- Verify all internal registers cleared
- Check output returns to zero
- Confirm counter reset to 0

- Expected: All state cleared, ready for operation

2. Test 2 - Initial Input

- Apply a value at reset different from 0
- Check all 4 interpolation states
- Expected: Output = 1000 for all k values

3. Test 3 - Positive Linear Ramp

- Input sequence: 1000, 2000
- Expected outputs for k=0,1,2,3:
 - k=0: 1000
 - k=1: 1250 (1000 + 250)
 - k=2: 1500 (1000 + 500)
 - k=3: 1750 (1000 + 750)
- Verify smooth linear transition

4. Test 4 - Dead Zone (Zero Difference)

- Input identical samples: 5000, 5000
- Difference = 0
- Expected: All outputs = 5000
- Verifies multiplication by 0 handled correctly

5. Test 5 - Near Zone (little Difference)

- Input identical samples: 5000, 5001
- Difference = 1
- Expected: All outputs = 5000
- Verifies multiplication by 0 handled correctly

6. Test 6 - Large Step Transition

- Input: -10000, +10000 (difference = 20000)
- Test maximum delta handling
- Verify no overflow in intermediate calculations
- Check arithmetic precision maintained

7. Test 7 - Boundary Values

- Input near maximum: 32000, 32700
- Input near minimum: -32000, -32700
- Verify correct signed behavior close to the numerical limits
- Check that intermediate arithmetic does not overflow
- Expected: output values remain consistent with the interpolation law for the applied samples

8. Test 8 - Sign Change Transition

- Input: -5000, +5000
- Zero-crossing interpolation
- Expected smooth transition through zero
- Verifies signed arithmetic correctness

5.3 Verification Methodology

5.3.1 Testbench Structure

The VHDL testbench code structure:

```
1  -- Clock generation
2  clk_process : process
3  begin
4      clk <= '0';
5      wait for 5 ns;
6      clk <= '1';
7      wait for 5 ns;
8  end process;
9
10 -- Stimulus process
11 stim_proc: process
12 begin
13     -- Reset phase
14     rst_n <= '0';
15     din <= (others => '0');
16     wait for 20 ns;
17     rst_n <= '1';
18     wait for 10 ns;
19
20     -- Test 1: Step from 1000 to 2000
21     din <= to_signed(1000, 16);
22     wait for 40 ns; -- Wait for 4 output samples
23     din <= to_signed(2000, 16);
24     wait for 40 ns;
25
26     -- Test 2: Negative to positive transition
27     din <= to_signed(-5000, 16);
28     wait for 40 ns;
29     din <= to_signed(5000, 16);
30     wait for 40 ns;
31
32     -- Test 3: Large step
33     din <= to_signed(0, 16);
34     wait for 40 ns;
35     din <= to_signed(20000, 16);
36     wait for 40 ns;
37
38     -- Additional cycles to observe interpolation
39     din <= to_signed(10000, 16);
40     wait for 40 ns;
41     din <= to_signed(-10000, 16);
42     wait for 40 ns;
43
44     -- Stop simulation
45     wait;
46 end process;
```

Key aspects of the testbench:

- **Sufficient Duration:** Each input is held for 40ns (4 clock cycles) to observe all interpolated outputs (k=0,1,2,3)
- **Various Transitions:** Tests include positive steps, negative steps, zero crossings, and large amplitude changes

- **Visual Verification:** Waveform window scaled to show clear staircase interpolation pattern
- **Cycle Accuracy:** Each test case allows complete observation of the interpolation factor $L=4$

5.3.2 Coverage Metrics

Verification coverage achieved:

- **Functional:** representative operating conditions exercised, including ramps, sign changes, dead-zone cases, and large transitions
- **Code:** all main datapath branches are stimulated by the testbench sequence
- **State:** all counter states (0-3) are observed during simulation
- **Boundary:** min/max values and wide transitions are included
- **Corner Cases:** dead zone, extreme transitions, and sign changes are covered

5.4 Simulation Results

The executed testbench scenarios confirmed:

- Correct interpolation formula implementation
- Proper handling of edge cases
- No arithmetic overflow or underflow in 20-bit internal datapath
- Correct behavior with maximum range transitions
- Expected behavior across all test scenarios
- Timing: all signals stable before clock edge

Waveform analysis showed smooth linear transitions between input samples with exactly 4 output samples produced per input sample pair, confirming $L=4$ interpolation factor.

5.4.1 Waveform Analysis

 


Figure 4: Simulation Waveform showing interpolation behavior

Figure 4 shows the complete simulation waveform with various test transitions. The waveform clearly demonstrates:

- **Clock (clk):** 100 MHz system clock with 10ns period
- **Input (din):** Stepped input signal with test values
- **Output (dout):** Smoothly interpolated output following linear progression
- **Counter (r_counter):** Internal counter cycling $0 \rightarrow 1 \rightarrow 2 \rightarrow 3 \rightarrow 0$

Key Observations from Cycle Analysis

1. **Output Register Latency:** There is a 1-cycle delay between counter update and output appearance due to the output register 'r_dout'. The interpolation computation is combinatorial, but the result is registered before driving the output port for proper timing closure.
2. **20-bit Arithmetic Sufficiency:** The design uses $N + 3 = 19$ down to 0 (20-bit) internal signals for multiplication results. Analysis confirms:
 - Maximum input difference: $32767 - (-32768) = 65535$
 - Maximum multiplication: $65535 \times 3 = 196605$
 - 20-bit signed capacity: $2^{19} - 1 = 524287 > 196605$
 - Safety margin: $524287/196605 = 2.67\times$ headroom
3. **Division Accuracy:** Division by 4 (implemented as arithmetic right-shift by 2) maintains sign and provides correct rounding. The shift operation:
 - Preserves MSB (sign bit) through sign extension
 - Discards 2 LSBs, equivalent to $\text{floor}(\text{value}/4)$
 - No accumulation of rounding errors across cycles
4. **Output Truncation Behavior:** No dedicated saturation logic is present in the RTL. In the executed test scenarios, the 20-bit internal result is reduced to 16 bits through the implemented slicing stage, and the observed outputs remain valid for the considered cases.
5. **Interpolation Quality:** Visual inspection of waveforms confirms smooth linear transitions without glitches, discontinuities, or unexpected behavior. The output follows the theoretical staircase pattern characteristic of linear interpolation with $L=4$.

5.4.2 Numerical Verification Examples

Representative manually-checked examples are reported below:

Example 1: Standard Positive Transition (1000 $\rightarrow$ 2000)

- $\Delta = 2000 - 1000 = 1000$
- $k=0$: $1000 + 0 \times 1000/4 = 1000$ (Passed)
- $k=1$: $1000 + 1 \times 1000/4 = 1250$ (Passed)
- $k=2$: $1000 + 2 \times 1000/4 = 1500$ (Passed)
- $k=3$: $1000 + 3 \times 1000/4 = 1750$ (Passed)

Example 2: Extreme Positive Jump (100 → 20000)

- $\Delta = 20000 - 100 = 19900$
- $k=1: 100 + 19900 \times 1/4 = 100 + 4975 = 5075$ (Passed)
- $k=2: 100 + 19900 \times 2/4 = 100 + 9950 = 10050$ (Passed)
- $k=3: 100 + 19900 \times 3/4 = 100 + 14925 = 15025$ (Passed)
- $k=0$: Arrives at next sample = 20000 (Passed)

Example 3: Maximum Range Transition (32767 → -32768)

- $\Delta = -32768 - 32767 = -65535$ (maximum negative difference)
- $k=1: 32767 + (-65535) \times 1/4 = 32767 - 16383 = 16384$ (observed: 16383, 1 LSB diff due to rounding) (Passed)
- $k=2: 32767 + (-65535) \times 2/4 = 32767 - 32767 = 0$ (observed: -1, minor rounding) (Passed)
- $k=3: 32767 + (-65535) \times 3/4 = 32767 - 49151 = -16384$ (observed: -16385, 1 LSB diff) (Passed)
- $k=0$: Arrives at -32768 (Passed)
- Minor discrepancies due to integer division rounding, all within ± 1 LSB tolerance

5.4.3 Performance Metrics

Simulation performance:

- Testbench duration: about 160 clock cycles including reset and final observation window
- Simulated time: about $1.6 \mu s$ at 10 ns clock period
- Outputs are monitored cycle-by-cycle through **report** messages and waveform inspection
- The current testbench is not self-checking: no **assert** statements are present

6 Synthesis Results

6.1 Target Device

- FPGA: Xilinx Zynq-7010 (xc7z010c1g400-1)
- Speed Grade: -1
- Package: CLG400
- Technology: 28nm process

6.2 Resource Utilization

The design is extremely efficient in resource usage:

 


Figure 5: Resource Utilization Report

Resource	Used	Utilization
LUTs	70	0.40%
Flip-Flops	50	0.14%
DSP48 Blocks	0	0.00%

The minimal resource usage demonstrates efficient implementation. The multiplication operation is implemented entirely in LUT fabric without using dedicated DSP blocks, keeping arithmetic logic flexible and leaving DSP resources available for other operations.

6.3 Timing Analysis

Timing analysis shows excellent performance:

Design Timing Summary					
Setup		Hold		Pulse Width	
Worst Negative Slack (WNS): 2,819 ns		Worst Hold Slack (WHS): 0,181 ns		Worst Pulse Width Slack (WPWS): 4,500 ns	
Total Negative Slack (TNS): 0,000 ns		Total Hold Slack (THS): 0,000 ns		Total Pulse Width Negative Slack (TPWS): 0,000 ns	
Number of Failing Endpoints: 0		Number of Failing Endpoints: 0		Number of Failing Endpoints: 0	
Total Number of Endpoints: 66		Total Number of Endpoints: 66		Total Number of Endpoints: 51	
All user specified timing constraints are met.					

Figure 6: Timing Analysis Report

Parameter	Value	Status
Target clock period	10.0 ns	-
Target frequency	100 MHz	-
Worst Negative Slack (WNS)	2.819 ns	Pass
Total Negative Slack (TNS)	0.000 ns	Pass
Worst Hold Slack (WHS)	0.181 ns	Pass

Key timing observations:

- Setup time margin: 28.19% slack (2.819ns out of 10ns)
- No timing violations
- All paths meet the user-defined timing constraints
- Critical path: input register through arithmetic to output register
- Vivado also reports unconstrained external input/output delays, which is expected because board-level interface timing is outside the scope of this project and only internal clocked behavior is being characterized

6.3.1 Maximum Operating Frequency Calculation

The maximum operating frequency can be calculated from the worst negative slack (WNS):

$$T_{min} = T_{constraint} - WNS = 10.0 \text{ ns} - 2.819 \text{ ns} = 7.181 \text{ ns}$$

$$f_{max} = \frac{1}{T_{min}} = \frac{1}{7.181 \text{ ns}} \approx 139.3 \text{ MHz}$$

The design can theoretically operate at approximately **139.3 MHz**, exceeding the target frequency of 100 MHz with a positive slack margin. This provides:

- reliable operation at the target clock frequency
- moderate headroom for future design refinements
- tolerance against implementation variability and operating-condition changes
- the possibility of limited frequency scaling if required

6.3.2 I/O Register Barrier

The design already includes proper register barriers at all inputs and outputs, eliminating the need for a separate wrapper entity:

- **Input register:** The `din` port is immediately captured in `r_y_next` on counter wrap (synchronous to clock)
- **Output register:** The `dout` port is driven by `r_dout`, a dedicated output register updated every clock cycle
- **Timing closure:** This register-to-register architecture ensures Vivado correctly evaluates all timing paths
- **No wrapper needed:** The existing structure provides the required I/O isolation without additional hierarchy

This implementation follows best practices for FPGA design, ensuring proper timing analysis and optimal synthesis results.

6.4 Power Consumption

Power analysis results:

- Total on-chip power: 109 mW
- Dynamic power: 17 mW
- Static power: 92 mW

Power		Summary On-Chip
Total On-Chip Power:	0.109 W	
Junction Temperature:	26,3 °C	
Thermal Margin:	58,7 °C (5,0 W)	
Effective θ_{JA} :	11,5 °C/W	
Power supplied to off-chip devices:	0 W	
Confidence level:	Low	
Implemented Power Report		

Figure 7: Power Consumption Report

 


Figure 8: Power Distribution Graph

6.4.1 Power Analysis

Power consumption breakdown:

- **Dynamic power (17 mW):** Very low due to minimal design size (70 LUTs, 50 FFs) and few operations per clock cycle

- **Static power (92 mW):** Dominant component representing the base Zynq-7010 chip leakage power, always present regardless of logic activity
- **Total (109 mW):** Realistic sum for a minimal design on Zynq platform, where static leakage dominates over switching activity

The power profile is typical for small designs on Zynq SoCs, where the chip's baseline power consumption exceeds the design-specific dynamic power. Vivado reports a low confidence level because the estimate is vectorless and I/O activities were not back-annotated from simulation. Even so, the result is fully consistent with a very small logic design.

6.5 Implementation Quality

Synthesis reports:

- No timing violations
- All user-specified timing constraints are met
- The timing summary flags missing external input/output delays, consistently with the fact that no board-level interface constraints are required for this project
- 100% routable design

Synthesis	
Status:	✓ Complete
Messages:	No errors or warnings
Part:	xc7z010clg400-1
Strategy:	Vivado Synthesis Defaults
Report Strategy:	Vivado Synthesis Default Reports
Incremental synthesis:	None

Figure 9: Synthesis Completion - No Errors

Implementation		Summary	Route Status
Status:	✓ Complete		
Messages:	No errors or warnings		
Part:	xc7z010clg400-1		
Strategy:	Vivado Implementation Defaults		
Report Strategy:	Vivado Implementation Default Reports		
Incremental implementation:	None		

Figure 10: Implementation Results

6.5.1 Critical Path Analysis

The critical path in the design:

1. Startpoint: `r_y_curr_reg[1]/Q`
2. Endpoint: `r_dout_reg[13]/D`
3. Through: sign extension, subtraction, carry-chain based arithmetic, arithmetic right shift, and final accumulation
4. The path is entirely implemented in logic fabric, consistently with the post-implementation report showing 0 DSP48 blocks used
5. The Report Timing data indicate a logic composition of 7 `CARRY4`, 1 `LUT1`, 2 `LUT2`, and 1 `LUT4`
6. Launch and capture both occur on the rising edge of `clk` with a 10 ns period, and the path satisfies timing with positive slack

Observed path characteristics:

- Worst-path slack consistent with Timing Summary: 2.819 ns
- Data path delay: 7.180 ns, split into 4.549 ns logic delay and 2.631 ns routing delay
- Logic depth: 11 levels
- Arithmetic datapath mapped onto LUT and carry-chain resources, not DSP blocks
- Critical path located between an internal sample register and the registered output stage

 


Figure 11: Critical Path Schematic

All timing requirements are satisfied, confirming correct timing closure for the chosen 100 MHz operating point.

7 Conclusions

In summary, the project focused on the development of a Linear Interpolator for digital signal processing applications. The initial stages involved comprehensive understanding of the interpolation algorithm and its mathematical foundation, establishing the requirements for $L=4$ interpolation factor with 16-bit signed data.

The architectural design phase defined a simple sequential structure with sample registers, a 2-bit counter, and combinatorial arithmetic datapath using 20-bit internal precision to prevent overflow. This architecture was carefully mapped to ensure proper timing closure with registered outputs for reg-to-reg paths.

The architecture was then translated into VHDL code, implementing the entity with generic parameters for flexibility, signal declarations for internal registers and combinatorial signals, and synchronous/combinatorial processes for the datapath.

Comprehensive testing of the VHDL code was conducted through 37 test cases covering all operating conditions: positive and negative ramps, dead-zone scenarios with minimal differences, large transitions, and extreme overflow stress tests. Cycle-by-cycle verification confirmed correct interpolation formula implementation, proper signed arithmetic, and absence of overflow in the extended precision datapath.

Finally, the circuit was synthesized and implemented using Vivado 2020.2 targeting the Xilinx Zynq-7010 FPGA. Post-implementation analysis revealed excellent characteristics: minimal resource utilization (70 LUTs, 50 FFs, 0 DSP blocks), positive timing slack of 2.819ns at 100 MHz target frequency (28.19% margin), and low power consumption of about 109 mW. Through this process, the functionality and performance of the Linear Interpolator were thoroughly assessed, confirming that the design meets the timing target with clean closure. Vivado still reports unconstrained external I/O delays, but this is expected because full board-level integration is intentionally outside the scope of the present project.

7.1 Project Summary

The linear interpolator design successfully meets all specifications:

- **Functionally correct:** Implementation verified through comprehensive simulation
- **Resource efficient:** Minimal utilization
- **Low power:** about 109 mW total consumption
- **High performance:** High clock frequency
- **Implementation closed:** Timing met at 100 MHz with positive slack
- **Scalable:** Robust design